

Application of Intersil Digitally Controlled Potentiometers (XDCP™) as Hybrid Analog/Digital Feedback System Control Elements

For the most part, the universe of feedback system design separates neatly into two fundamental design paradigms: analog-based designs and digital-based designs. Both design strategies are characterized by advantages and liabilities that generally make one or the other a clearly superior choice for any given application. Pure analog designs, for example, tend to display design simplicity and low development costs that play well in the context of smaller system applications. Digital-based designs, by contrast, have essentially unlimited flexibility in computation of the feedback function and therefore dominate in more complex feedback applications in which higher development costs (generally including software implementation) can be justified. Sometimes, a feature of particular utility in digital designs is the availability of digital memory with its ability to store feedback parameters for arbitrary lengths of time without drift. This makes possible a variety of system solutions including multiple system operating modes in which feedback values can be acquired in some modes and then applied in others.

But what about feedback systems that lie in between these clear opposites? What about, relatively simple cost-sensitive applications that would benefit from functions that are difficult to implement in analog circuits and would therefore require digital techniques?

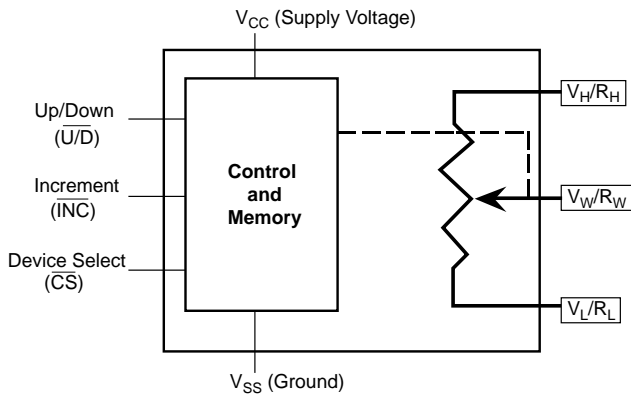


FIGURE 1. DIGITALLY-CONTROLLED POTENTIOMETER

A basis for a useful middle ground between the extremes of pure analog or pure digital feedback designs is offered by an inexpensive component: the Intersil 3-wire digitally controlled potentiometer. Figure 1 illustrates the architecture of the 3-wire XDCP. The 3-wire XDCP is seen to comprise a digital input and an analog output interface. The 3-wire XDCP digital input interface consists of a bidirectional counter controlled by (direction [U/D], clock [INC] inputs, and chip select/EEPROM-store [CS] logic signals). The XDCP analog output interface consists of the digitally controlled variable resistance potentiometer element.

A generalized basic conceptual topology representative of feedback control systems based on the 3-wire XDCP is illustrated in Figure 2. It comprises six design elements:

A. The XDCP Error Integrator. During the feedback process, the XDCP closes the feedback loop by accumulating successive samples of the system state in its up/down control counter.

B. Clocking Oscillator. The oscillator controls the rate of feedback sampling. Therefore, selection of the oscillator period must be based on consideration of both the minimum response time of the XDCP (< 500µs for typical Intersil parts) and of the rest of the feedback system as determined by such factors as the gain-bandwidth products of the op amp and comparator. Appropriate oscillator periods will typically lie in the range of 1 to 100 milliseconds.

C. Analog/Digital Feedback (Voltage Comparator). Conversion between the analog state of the output node and the digital U/D XDCP input is the traditional role of the analog comparator. However, the flexibility of the CMOS logic inputs of Intersil XDCPs often makes it possible to substitute a simple passive voltage-translation network, as illustrated in the design applications to follow.

D. Digital/Analog Feedback (Resistance Element Circuitry). Closure of the feedback loop is achieved by incorporation of the variable resistance element of the XDCP into the active circuitry of the rest of the feedback system.

E. Intermittent Feedback Control Circuitry (Selectable Operating Modes). Some uniquely versatile XDCP-based feedback control applications derive their utility from the ability to implement multiple operation modes in which circuit setpoints (e.g. precision op amp offset null) derived from one operating mode (e.g. autonull mode) are retained in XDCP memory and used in a subsequently selected system mode (e.g. DC amplification). Control and selection of such system operating modes is easily achieved through the use of inexpensive, logic-compatible, CMOS analog switch elements such as the 74HC4053.

F. Operational Amplifier. Essentially all precision analog systems that can benefit from XDCP-based feedback designs will incorporate at least one monolithic op amp. Selection of a suitable (e.g. adequate gain, bandwidth, DC accuracy) op amp is therefore an important step in the feedback system design process.


Figure 2's conceptual topology has been utilized to advantage in a variety of real-life applications. Examples include:

**Auto-Nulling Delta-T Thermometer**

Some precision temperature measurement applications, such as acquiring the temperature rise of a heatsink in response to a thermal load, are inherently concerned with temperature change relative to an initial value rather than absolute temperature. In such applications, important improvement in measurement resolution can be gained from the scale expansion made possible by acquisition of the initial baseline temperature and subtracting it from subsequent measurements before analog to digital conversion. Figure 3 presents an auto-nulling thermometric circuit that performs this function automatically using digitally controlled potentiometers as the baseline temperature memory.





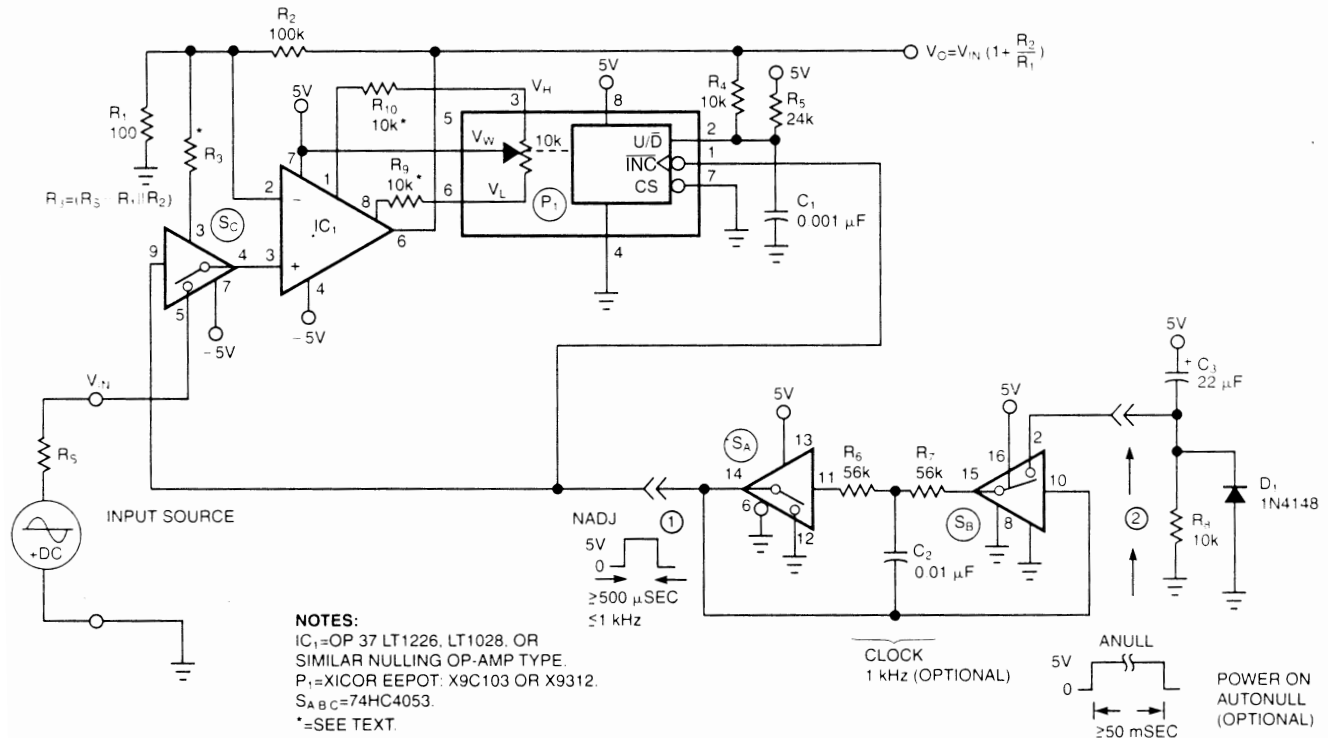

**FIGURE 4. HAVE YOUR CAKE (HIGH SPEED) AND EAT IT (LOW DC ERRORS) TOO, WITH THIS AUTONULLING CIRCUIT, USING A DIGITALLY CONTROLLED POTENTIOMETER**

Although Figure 4 shows an LT1226, the circuit works without modification with an OP37 and LT1028. The circuit is also pin-compatible with the popular LT1128, OP07, OP77, OP177, and μ725 op amps. With these op amps, however, the circuit may require a slower NADJ clock rate and a longer nulling interval (increase C2 and C3), because of the lower gain-bandwidth product of these compensated types. The circuit can accommodate many other op-amp types with a simple change of pin connections. The circuit can handle 15V positive-rail operations by substituting an X9312 for the X9C103 with no other changes.

### Power Amplifier Biasing

The day may be near when every amplifier application can be served simply by finding the right off-the-shelf stand-alone chip. But for now, many jobs require that even the best monolithic devices be supplemented with a sprinkling of active discrete devices. One such category of application is the high-output-current, high-frequency buffer amplifier in Figure 5.

Of course it's simplicity in itself to add an arbitrary amount of muscle to a "milquetoast" op amp by following it with a class AB complementary bipolar emitter-follower or FET source follower pair like Q1 and Q2 in Figure 5. Many successful driver designs are based on just this elementary topology. But all such designs must confront the problem of stable DC biasing of the follower while avoiding unconscionable amounts of quiescent power draw and unbearable levels of harmonic distortion. This is a problem fraught with the classic twin-design-bogeymen of thermal runaway and cross-over distortion.

The new solution to this old puzzle described here comprises an automatic bias adjustment loop consisting of an Intersil digital potentiometer P1, International Rectifier photovoltaic optoisolator O1, CMOS switches S1-S3, and Linear Technology op amps A2-3. The resulting adjustment loop includes two modes of operation selected by the CMOS/TTL-compatible ADJ input.

When ADJ = 0, S3 closes a normal feedback loop around A1 and the Q1/Q2 pair thus forcing the circuit to become a fairly normal gain of -5 amplifier with a bandpass of DC to 10 MHz, full power bandwidth (limited by A1 slew) of 5 MHz, and output limits of ±10V and ±10A. Harmonic distortion over the full operating range is minimized by the impressive GBW of capacitive-load-compatible A1 combined with stable quiescent biasing of the Q1/Q2 pair to a thrifty no signal value of 50 mA. The trick behind these performance numbers is the way an appropriate bias level for the follower is achieved, one that's independent of temperature and component tolerance variations.

To understand how this is done, consider how the circuit rearranges itself when ADJ = 1 causes S3 to disconnect A1's input from the signal source and substitute a ground reference. Simultaneously, the S1/S2, 20-Hz multivibrator is enabled and begins clocking P1. In response, P1 begins to vary the input to A3, which then services the control current into O1 and thus the net gate bias voltage at the follower MOSFETs.

This action combines with A2 to establish a feedback loop, which tends to drive the follower pair to the desired zero-signal bias. This action occurs because if the follower bias current  $I_Q$  is less than 50 mA, then the drop across R3 will be less than the drop across R4. As a result, A2 drives the Up/Down input of P1 high (up). Therefore, on the next negative transition of the clock, the VV terminal of P1 will make one step toward the VH terminal. This increases the drive to C1 which ups the follower bias.

If  $I_Q$  is more than 50 mA, then A2's output state will reverse, causing P1 to step VV toward VL and decrease the follower quiescent bias. Consequently, after a maximum of 5 seconds and 99 multivibrator cycles, the follower bias will have been forced to converge to the bias level set by the R4/R3 ratio. ADJ may then be reset to zero for normal amplifier operation; the final bias setting will be retained by P1 until either power is removed or a new ADJ cycle initiated. Thermal coupling between D1/Q1 and D2/Q2 improves overall bias stability between adjustment cycles.

Although illustrated with  $\pm 15\text{-V}$  supplies, the unique "Over-The-Top" input topology of A2 is compatible with  $V_+$  voltages as high as 36 V (but be careful to observe A1 limitations). Also, there is no requirement that the  $V_+$  and  $V_-$  voltages be symmetrical. Many variations are possible when selecting A1 and the follower MOSFETs to achieve different combination of output capabilities.

### Proportional-Integral Thermostat

A classic scheme for precision temperature control is the proportional-integral or "P/I" algorithm. In this method, the heater control equation consists of two terms. One term (P) is proportional to the instantaneous error differential between sensor and setpoint temperatures. The other (I) is proportional to the time integral of the error. P/I controllers characteristically have reasonably good dynamic response due to the proportional feedback term, nominally zero steady-state error thanks to the error integration term, and relatively simple loop optimization because only three adjustments (setpoint, proportional gain, and integrator time-constant) are involved in the setup process.

The simplicity of the P/I feedback algorithm argues for a similarly simple analog-based controller design. But some temperature-control applications involve long time-constants (running to minutes and hours) and often must live in hostile (hot and contaminated) industrial environments. These gremlins combine to make analog long-time-constant circuits problematic with their high impedances and nano-ampere signal currents. This is so because nasty ambients exaggerate the leakage and bias currents of op amps, integrator capacitors, and even circuit boards.

The controller shown in Figure 6 achieves adequate time-constants without the delicate high-impedance analog circuits. It uses Intersil's X9C103 digitally controlled potentiometers as feedback elements together with the Linear Technology LTC1040 sampled comparator.

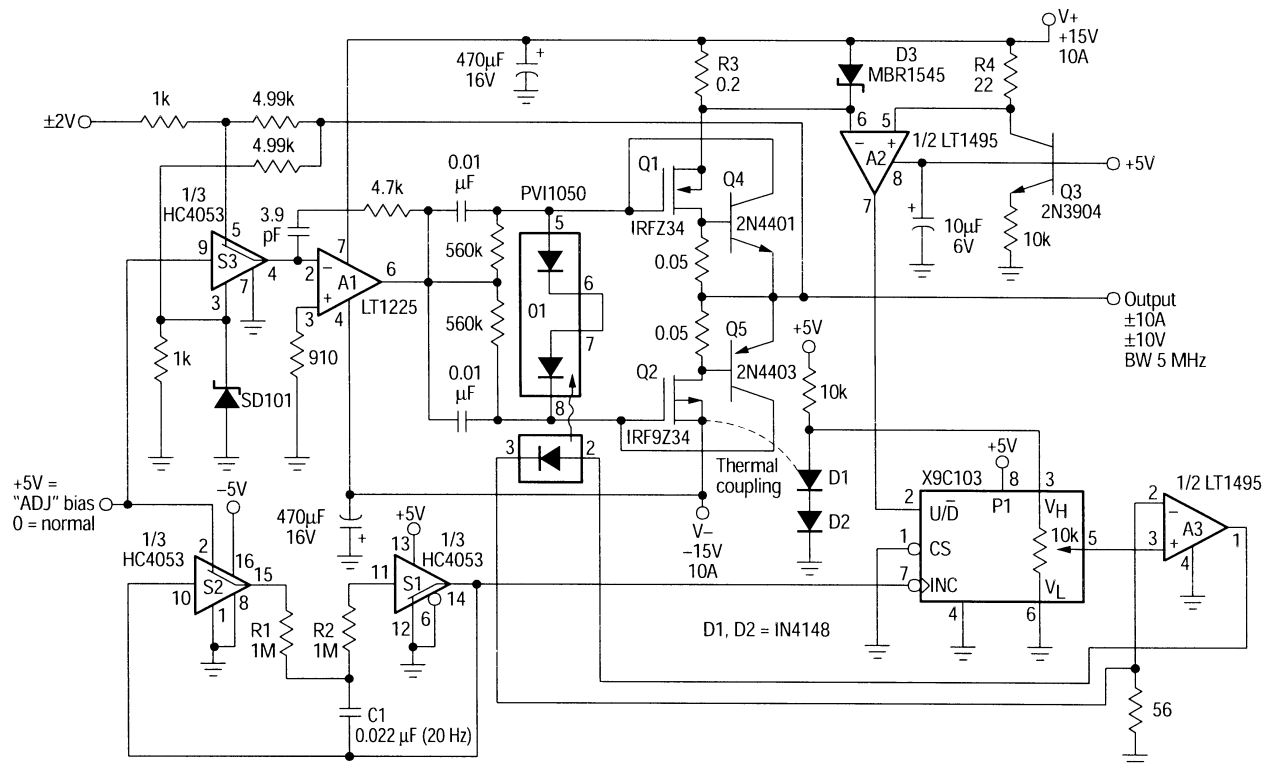


FIGURE 5. THIS HIGH-OUTPUT-CURRENT, HIGH-FREQUENCY BUFFER AMPLIFIER USES AN AUTOMATIC BIAS ADJUSTMENT LOOP, UTILIZING AN INTERSIL DIGITAL POTENTIOMETER P1, TO MINIMIZE HARMONIC DISTORTION WHILE DRAWING A THRIFTY NO-SIGNAL SUPPLY CURRENT OF ONLY 50 mA



Controller operation is based upon a positive-temperature-coefficient (3850 ppm/°C) platinum RTD sensor arranged in a standard ratiometric bridge with reference resistors R1, R3, and R5, and setpoint pot R4. Aiding controller stability and precision is high level ( $\approx 5$  mA) bridge excitation. It produces a relatively large 1.7 mV/°C RTD output signal that competes well against noise pickup and thermal-EMF error sources. Typically, such a high RTD drive level would threaten to produce large and unacceptable sensor self-heating errors. But in this case, sensor excitation is pulsed (80 $\mu$ s) under control of the LTC1040. This keeps average sensor dissipation duty factors low ( $\approx 1\%$ ) and self-heating error inconsequential.

On each measurement cycle, A1's lower input pair samples the bridge output. Depending on the result of the comparison, they tend to drive the pin 4 output bit to 0 or 1, as the bridge reports an RTD-setpoint differential that's negative or positive. Thus the solid-state relay (SSR) and heater will most likely turn on when the temperature is low and off when it is high.

To make the resulting on/off heater drive have an average duty-factor that is nicely proportional to the magnitude of the temperature error signal and not just a simple "bang-bang" relationship, the bridge output voltage is summed with a triangular dither signal produced by P2. The combination of P2 and U2

causes P2 to output one full triangular dither waveform every 128 measurement cycles.

Thermal inertia of the heater and the thermal load averages over the heater cycle rate (1 Hz in this example). Consequently, suitable selection of the R6-C1 oscillator RC will avoid significant temperature ripple. R2 adjusts the amplitude of the P2 dither signal and thereby sets the effective controller P-term gain that relates heater duty factor to temperature error to get adequate control loop "stiffness" without oscillation.

Meanwhile, error integrator A2 + P1 also samples the temperature difference signal. The integration sampling frequency, and, therefore, the integrator time constant, is set by the choice of which U2 output bit is connected to P1's clock. This arrangement causes the integrator to take one step in the direction of zero setpoint error every 1, 2, 4, 8, 16, 32, 64, or 128 heater dither cycles. As a result, it gradually converges on zero temperature error.

Selecting the right U2 bit sets the integrator time constant anywhere from one minute to more than two hours, and can thus accommodate even the longest generally encountered control-loop thermal time delays.

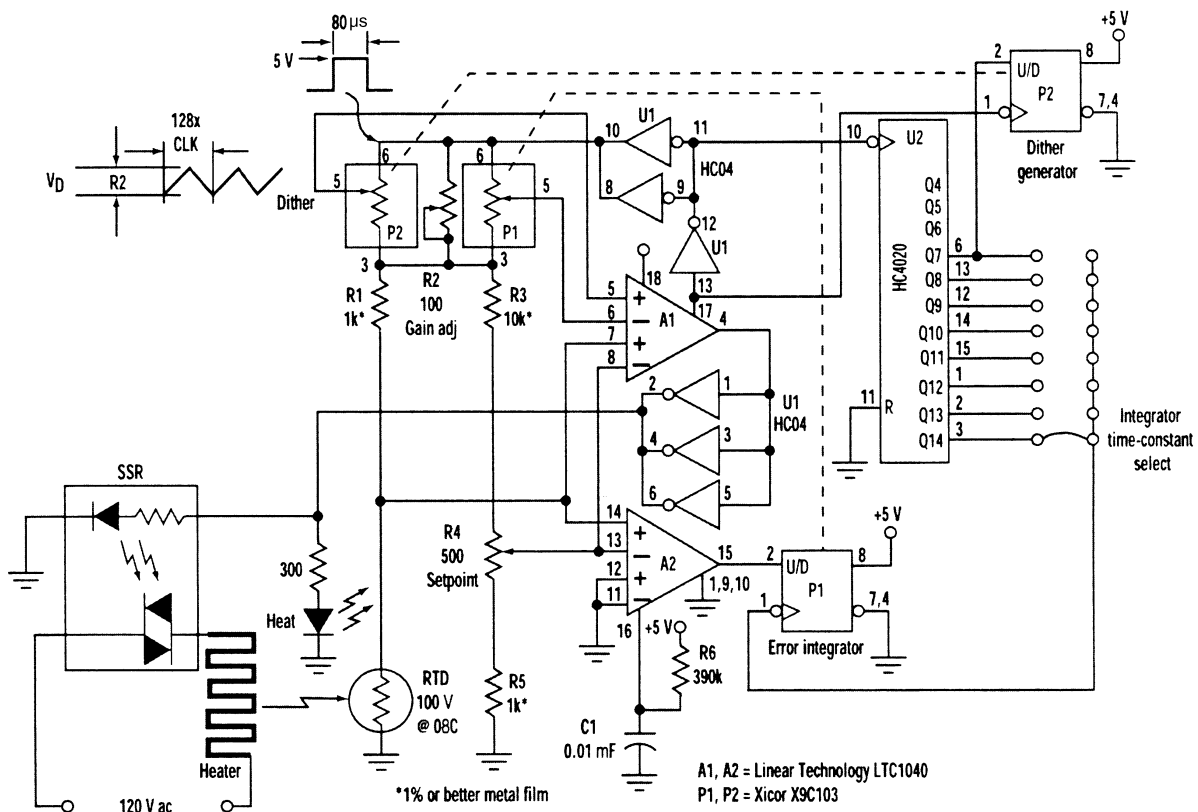


FIGURE 6. THIS CONTROLLER ACHIEVES EXTENDED TIME CONSTANTS WITHOUT DELICATE HIGH-IMPEDANCE ANALOG CIRCUITS BY USING INTERSIL'S X9C103 DIGITALLY-CONTROLLED POTENTIOMETERS AS FEEDBACK ELEMENTS, COMBINED WITH LINEAR TECHNOLOGY'S LTC1040 SAMPLED COMPARATOR

## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.  
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.  
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.  
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.  
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.  
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



### SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

**Renesas Electronics America Inc.**  
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.  
Tel: +1-408-432-8888, Fax: +1-408-434-5351

**Renesas Electronics Canada Limited**  
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3  
Tel: +1-905-237-2004

**Renesas Electronics Europe Limited**  
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.  
Tel: +44-1628-651-700, Fax: +44-1628-651-804

**Renesas Electronics Europe GmbH**  
Arcadiastrasse 10, 40472 Düsseldorf, Germany  
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

**Renesas Electronics (China) Co., Ltd.**  
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China  
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

**Renesas Electronics (Shanghai) Co., Ltd.**  
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China  
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

**Renesas Electronics Hong Kong Limited**  
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong  
Tel: +852-2265-6688, Fax: +852-2886-9022

**Renesas Electronics Taiwan Co., Ltd.**  
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan  
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

**Renesas Electronics Singapore Pte. Ltd.**  
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949  
Tel: +65-6213-0200, Fax: +65-6213-0300

**Renesas Electronics Malaysia Sdn.Bhd.**  
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia  
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

**Renesas Electronics India Pvt. Ltd.**  
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India  
Tel: +91-80-67208700, Fax: +91-80-67208777

**Renesas Electronics Korea Co., Ltd.**  
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea  
Tel: +82-2-558-3737, Fax: +82-2-558-5338