

Introduction

The minimum feature size of the MOS transistor has been greatly reduced since its invention just a few decades ago. Reductions in gate oxide thickness, channel length and width have been responsible for a revolutionary reduction in overall circuit size and power consumption. As the gate oxide thickness decreases the maximum allowable power supply voltage decreases; channel length and width reductions provide smaller and faster device performance. These device enhancements have afforded the development of high frequency CMOS rail-to-rail I/O amplifiers in answer to the modern system designers increasing demand for analog circuits capable of operation at the same low supply voltage as their digital counterparts.

This paper addresses the important issues uniquely related to the new generation of CMOS rail-to-rail amplifiers. Beginning with a general discussion and description of classic voltage feedback and current feedback amplifier circuit topologies and the most common causes of feedback

amplifier oscillation. Then the CMOS rail-to-rail amplifier circuit is divided into 4 basic blocks for analysis and discussion; input, intermediate gain, output and feedback network stages. The frequency dependent gain and phase shift of each stage will be presented, after which a complete system simulation of all 4 basic circuit blocks will be presented and discussed. The second section of this appnote will present and discuss the mechanism, trade-offs and benefits of 3 practical solutions to the amplifier oscillation issue.

Voltage Feedback Amplifier

Figure 1 shows a simplified schematic of the EL5157, a very popular high bandwidth voltage feedback amplifier. A classic differential input stage drives the folded cascode second stage, which converts the differential voltage of the input stage into a current at the high impedance gain node where it is realized as the high voltage gain of the amplifier. Essentially, the output impedance of the second stage current source becoming an output signal at the high

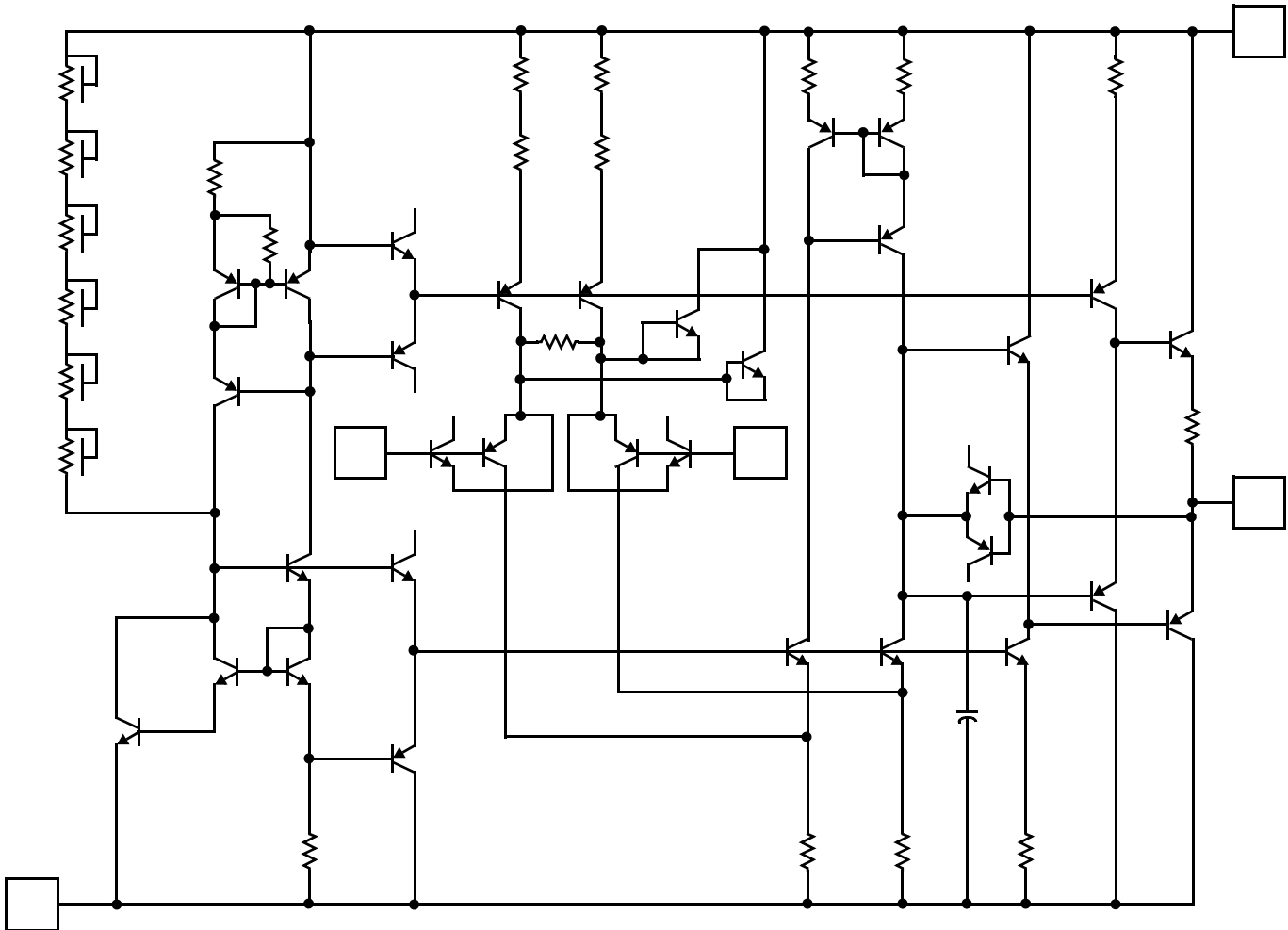


FIGURE 1. VOLTAGE FEEDBACK AMPLIFIER

impedance node multiplies any current difference occurring in the signal-path transistors. The output stage is a push pull class AB buffer and simply buffers the high voltage gain to the single ended output of the amplifier.

Output Inductance

An inductor is an electrical component with frequency dependent impedance characteristics; an inductor exhibits low impedance at low frequencies increasing to higher impedance at higher frequencies. While the "ideal" operational amplifier output impedance characteristic is zero the output impedance of "real" amplifiers is inductive and like the inductor increases with increasing frequency. The output impedance of the EL5157 is shown in Figure 2. A common challenge in applications using operational amplifiers is driving a capacitive load. A challenge because the inductive output of the op amp in conjunction with the capacitive load creates an LC resonant tank topology where the capacitive load reactance in conjunction with the inductive drive impedance results in extra phase lag when feed back is closed around the loop. Decreasing phase margin introduces the possibility of amplifier oscillation. When oscillating, the amplifier becomes very hot and can self-destruct. There are a couple of very well known solutions to this challenge. 1) The simplest solution is the addition of a resistor in series with the output to force the feedback to come from the amplifier's direct output while isolating the reactive load. The trade off of this method is the sacrifice of a small amount of the output voltage swing across the load. 2) Another straightforward solution is the application of a "snubber network". The snubber is a resistor and capacitor placed in parallel with the capacitive load providing resistive impedance across the load to diminish the output phase shift; providing additional stability.

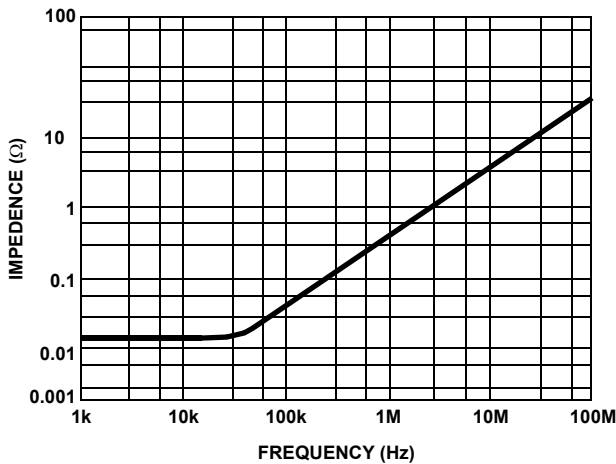


FIGURE 2. EL5157 OUTPUT IMPEDANCE

Current Feedback Amplifier

While current mode feedback operational amplifiers have been around for a long time, their high slew rate, high bandwidth and low distortion is responsible for their current popularity with ADSL systems and HDTV application designers.

Figure 3 shows a simplified drawing of a current mode feedback amplifier (CFA) EL5160. The +input is high impedance and buffered directly to the -input through transistors Q₆ & Q₇ and Q₁₀ & Q₁₁. It is this very low impedance of the -input stage that differentiates CFA and voltage mode feedback topologies and provides the CFA with unique advantages. Q₇ and Q₁₁ drive the current mirrors in the signal path of the high impedance node at the base of Q₈ and Q₁₂. These current mirrors supply current on demand to the high impedance node from the power supply providing the CFA an extremely high slew rate. The voltage level at this high impedance node is buffered to the output by emitter followers Q₉ and Q₁₃. Feedback connected from the output to the negative input forces the -input current to zero. A feedback resistor or resistor divider connected from output to the negative input converts the error voltage (voltage difference between V_{OUT} and V_{IN-}) into an error current. The amount of feedback is determined by the feedback resistor value. Every current feedback amplifier specifies an optimal feedback resistor value for highest bandwidth while maintaining stable operation. If feedback resistor smaller than the specified resistor is used, oscillation becomes a possibility. The CFA is also called a transimpedance amplifier because any change in the -input current results in change in output voltage.

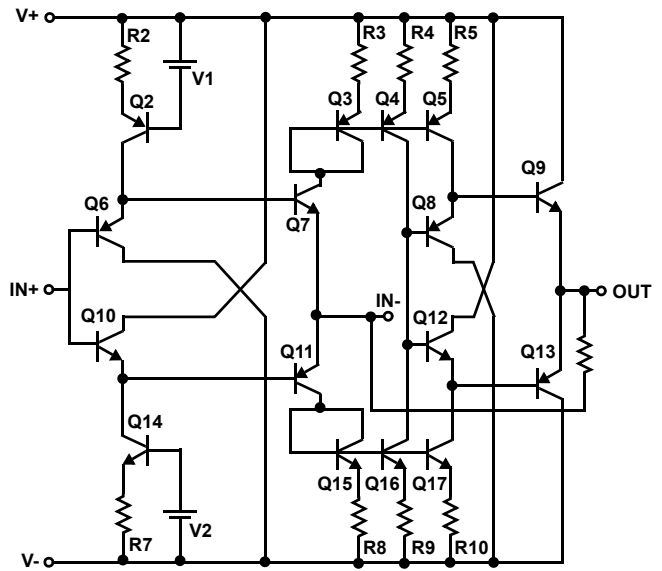


FIGURE 3. CURRENT FEEDBACK AMPLIFIER SIMPLIFIED SCHEMATIC


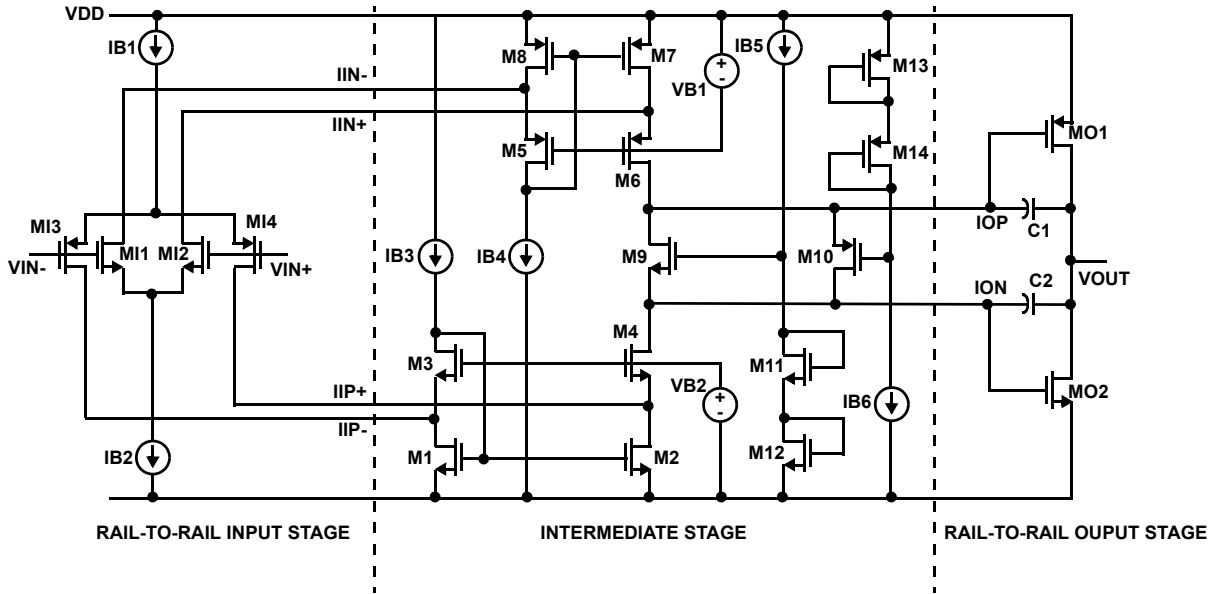


FIGURE 4. SIMPLIFIED SCHEMATIC OF A CMOS RAIL-TO-RAIL I/O AMPLIFIER

CMOS Rail-to-Rail Input/Output Amplifier


The simplified schematic of a CMOS rail-to-rail I/O amplifier, EL5411 is depicted in Figure 4. Consists of 3 stages - rail-to-rail input stage, intermediate gain stage and rail-to-rail output stage. The input stage is differential voltage input and differential current output. Its bandwidth extends to over 320MHz. The majority of the phase shift occurs over 100MHz beyond the bandwidth of the amplifier translating into generous phase margin. The gate capacitance of the differential input stage MOS transistors and package lead capacitance combine for 2.5pF of amplifier input capacitance. Where as the dominant pole of this topology is set by internal compensation capacitors C₁ and C₂. This stage converts differential current into differential voltage at the output; so we have differential voltage input and single ended output. To simplify analysis, we assume the input stage is a differential voltage buffer with unity gain and the voltage gain of the gain stage is 50dB with the dominant pole occurring at 11kHz. The output stage is rail to rail topology utilizing transistors connected in common source configuration. Unlike source follower buffer output stages, the large gain of the common source output stage changes with the output-loading resistor while the bandwidth changes with the output loading resistor and load capacitance. The complete amplifier open loop frequency response shown above is a combination of input, gain and output frequency responses. The 150pF loading capacitance reduces the bandwidth of the output stage resulting in an overall system bandwidth decrease and phase margin reduction of 17°, a marginally stable condition. When in unity gain configuration the buffer configuration with V_{out} and V_{in-} directly shorted, the amplifier can drive 150pF and 200Ω load while remaining stable. The trouble occurs when resistor is placed in the feedback path.

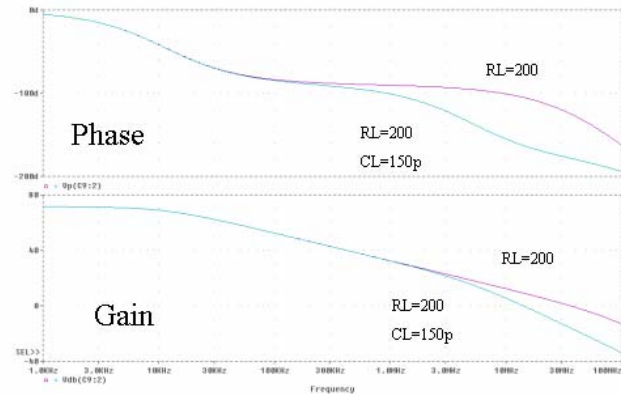

R _{LOAD}	C _{LOAD}	GBWP	PHASE MARGIN
200Ω	NO	35MHz	56°
200Ω	150pF	14MHz	17°

FIGURE 5. CMOS RAIL TO RAIL AMPLIFIER OPEN LOOP RESPONSE

F is the feedback resistor, R_G is the gain resistor. If we select reasonable component values -- R_F = 3k and R_G = 8.3k. the feedback network combined with the 2.5pF capacitor at the negative input forms a low pass network from the amplifier output to the negative input. The frequency response of this feedback network shows -45° phase shift at 30MHz. The frequency response of the complete system including feedback network is shown in Figure 6. The feedback network reduces the overall system gain slightly because of the extra pole introduced by the feedback network. The most negative impact of this additional pole is that it reduces the phase by a significant amount. Under 150pF and 200Ω loading condition, the system with R_F = 3k, R_G = 8.3k feedback network has 11.5MHz gain bandwidth product and 0° phase margin and the system oscillates.

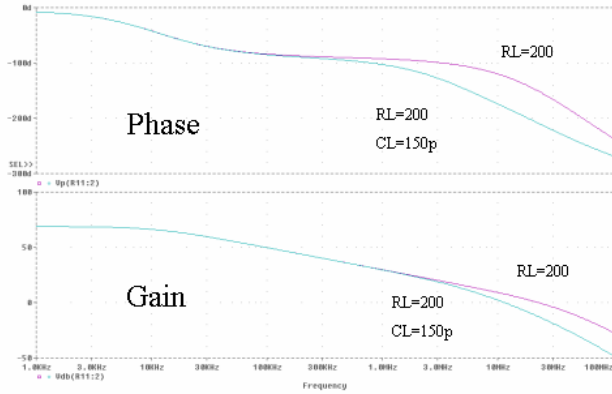


R _{LOAD}	C _{LOAD}	GBWP	PHASE MARGIN
200Ω	NO	22.5MHz	30°
200Ω	150pF	11.5MHz	0°

FIGURE 6. COMPLETE LOOP FREQUENCY RESPONSE WITH 3K R_F AND 8.3K R_G FEEDBACK NETWORK

Reduce feedback resistor value to minimize the impact of C_{in}

The phase shift and the loss of phase margin is caused by the action of the R_F-R_G-C_{IN} low pass filter. Reducing the R_F and R_G values will shift this low pass filter pole to a higher frequency (>30MHz). In the above example, as R_F and R_G values decrease 3X the pole moves from 30MHz to around 90MHz. Figure 7 shows the complete system frequency response with 3X smaller R_F and R_G values. This is a very nice solution because the gain bandwidth product changes very little while phase margin improves significantly. Under 200Ω and 150pF condition, the phase margin increases to 14° from 0°. The system is now stable. The minor trade-off with this solution is the amplifier now drives a 1k feedback, resulting in slightly increased power dissipation.

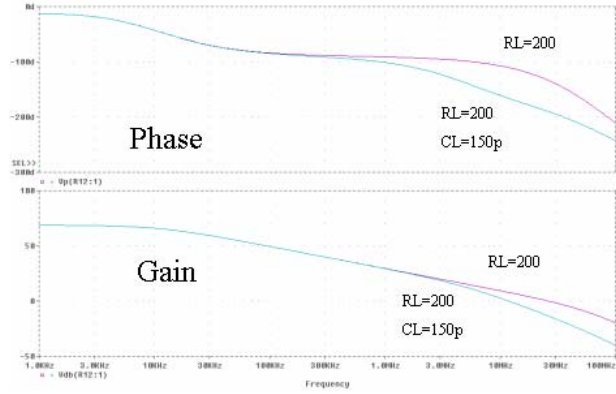


R _{LOAD}	C _{LOAD}	GBWP	PHASE MARGIN
200Ω	NO	25.7MHz	47°
200Ω	150pF	11.7MHz	14°

FIGURE 7. COMPLETE LOOP FREQUENCY RESPONSE WITH LOWER R_F AND R_G VALUES

Place C_{comp} in parallel with R_F

This solution introduces a small compensation capacitor (C_{comp}) in parallel with R_F without changing the values of R_F and R_G. The C_{comp} capacitor introduces a phase lead to cancel out the phase lag caused by C_{in}. The complete system frequency response with 5pF C_{comp} capacitor is shown in figure 8. The gain bandwidth product changes very little, however, the phase margin improves significantly. Under 200Ω and 150pF condition, the phase margin increases to 19° from 0°. The system is now stable with an additional C_{comp} capacitor while maintain minimum power consumption.

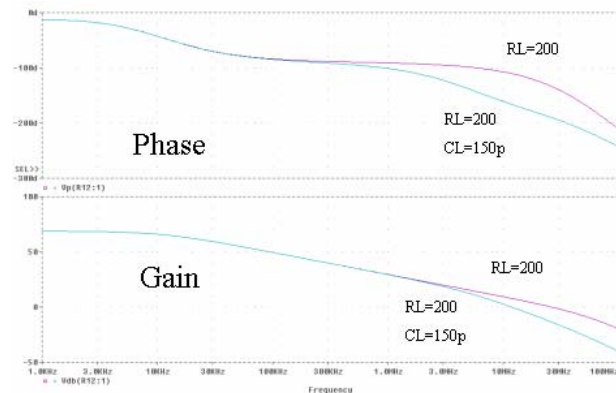


R _{LOAD}	C _{LOAD}	GBWP	PHASE MARGIN
200Ω	NO	25.7MHz	47°
200Ω	150pF	11.7MHz	14°

FIGURE 8. COMPLETE LOOP FREQUENCY RESPONSE WITH 5pF C_{COMP}

Increase close loop gain

The solution utilizes a large R_F and R_G ratio to increase closed loop gain. We use 43k R_F and 8.3k R_G in our example. The gain and phase curves of this R_F and R_G combination show a pole at 9MHz with -16dB attenuation. The -16dB attenuation reduces the overall system gain by 16dB. The complete system frequency response with large close loop gain is in Figure 9. The overall system open loop gain reduces by 16dB, decreasing to 54dB from 70dB. As a result, the gain bandwidth product decreases to around 5MHz. Therefore, the phase margin improves significantly. Under 200 Ω and 150pF condition, the phase margin increases to 20° from 0°. The system is now stable by sacrificing bandwidth.

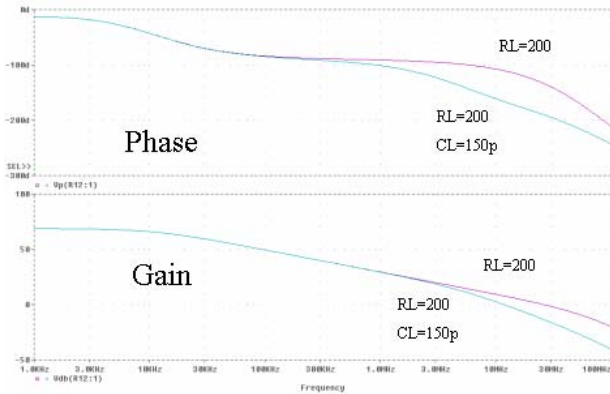

R_{LOAD}	C_{LOAD}	GBWP	PHASE MARGIN
200 Ω	NO	25.7MHz	47°
200 Ω	150pF	11.7MHz	14°

FIGURE 9. COMPLETE LOOP FREQUENCY RESPONSE WITH LARGE CLOSE LOOP GAIN

Unlike traditional amplifiers, the common source output stage of the rail-to-rail I/O amplifier has gain and bandwidth more sensitive to resistive a capacitive loading. The bandwidth variation along with the input capacitance significantly impacts amplifier stability. This application note has presented circuit designs of a rail-to-rail input and output CMOS amplifier where 3 possible solutions to the challenge of reducing amplifier instability have been discussed

1. Feedback resistor value reduction to minimize the impact of C_{IN} .
2. Introduction of a C_{comp} in parallel with R_F .
3. An Increase of closed loop gain.

R_{LOAD} (Ω)	C_{LOAD} (pF)	GBWP (MHz)	PHASE MARGIN
200	No	6.7	52.3
200	150	4.5	20

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338