

Introduction

The circuit in Figure 1 transmits 200MHz (-3dB bandwidth) video signals while stripping off the sync pulse and performing DC restoration. It is configured for a typical video cable driver application driving a double-terminated 75Ω load, where the EL8102 (IC3) is configured for a gain of +2 to ensure unity gain throughout.

Sync Stripping

In component video systems it is frequently necessary to remove the sync pulse from an RGB signal. Sync is often combined with one or more of the red, green, and blue video signals in video distribution amplifiers, routers and switchers to decrease the number of input and output channels required in a switching network. In many applications, however, as the video signals exit the switching network the sync pulse must be removed.

The EL8102 video op amp is specially designed to perform sync stripping. Its open emitter NPN output forms an emitter-follower with the load resistor, and passes the active video signal while virtually eliminating the negative sync pulse (see Figure 2). Residual sync of the EL8102, defined as the remainder of the original -300mV sync pulse, referenced to ground, is only 8mV at the cable output. A particular advantage of sync stripping with the EL8102 is the resultant larger (by 0.7V) output voltage swing, compared to simply using a wideband video op amp with an external emitter-follower.

Because the EL8102 contains no active pull-down, output linearity degrades as the signal approaches ground. To deal with this a 6.8kΩ pull-up resistor (R₈) and a 75Ω pull down resistor (R₁₀) on the output ensure a fixed positive voltage offset, in this case +50mV. This offset was arbitrarily chosen as a good compromise between linearity near the DC level and minimum residual sync. Increasing R₈ decreases residual sync, at the expense of linearity. Conversely, decreasing R₈ decreases linearity error, but increases residual sync. Other applications benefitting from sync removal are HDTV systems and video digitizing circuits. Consider a typical 1V_{P-P} RGB video signal with a -300mV sync pulse and +700mV video data. By stripping off the unwanted sync pulse and digitizing only the active video, designers can use the full dynamic range of the A/D converter for the +700mV video data. This results in a 30% increase in resolution using the same A/D converter.

DC Restore

Another common video function is DC restoration, used when AC coupled signals have lost their DC reference and must have it periodically reset in order to retain brightness information.

This circuit accomplishes DC restoration using a CA5260 dual op amp (IC1a, IC1b) coupled with a sample-and-hold circuit based on the 74HC4053 switch (IC2). V_{IN}, consisting of the input video signal and a DC offset (V_{DC}), is routed to the non-inverting input of the EL8102 (IC3). The EL8102 is configured in a gain of +2 (to compensate for the attenuation resulting from double terminating the cable), which would result in an output of 2 x V_{IN} = (2 x Video + 2 x V_{DC}), if not for the DC restore circuit.

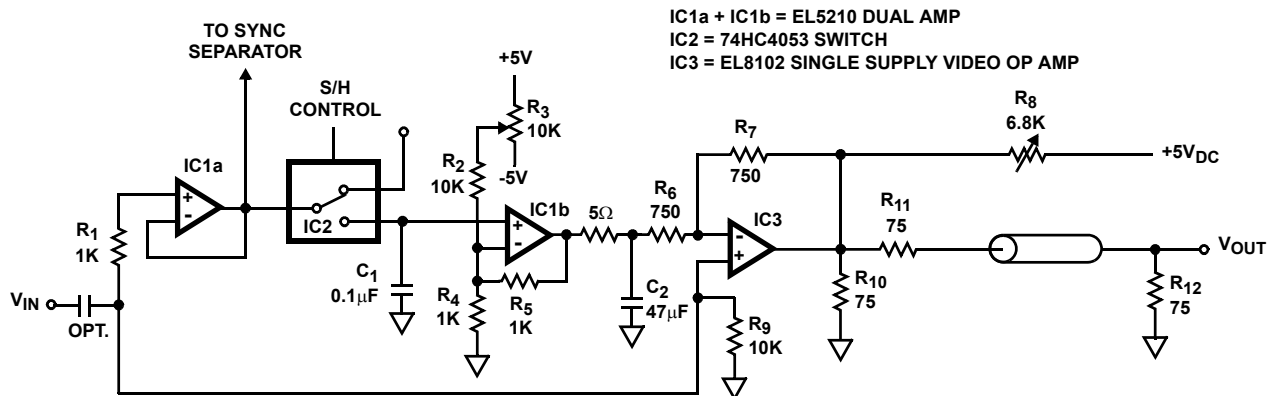


FIGURE 1. EL8102 BASED VIDEO AMPLIFIER WITH SYNC STRIPPING AND DC RESTORE

V_{IN} also travels through half of the dual CA5260 amplifier to the sample-and-hold circuit, where the $0.1\mu\text{F}$ capacitor (C_1) is the hold capacitor. The sample-and-hold control is triggered by a back-porch pulse from a sync separator or by a horizontal video blanking signal. The DC output signal (V_{DC}) from the sample-and-hold circuit is then amplified at a gain of +2 by the second op amp (IC1b); the gain is required because V_{DC} is input to the EL8102s inverting input which provides only a gain of -1, but as discussed earlier, the output contains a term of $2 \times V_{DC}$. Thus $2 \times V_{DC}$ is summed into the EL8102 inverting input, is subtracted from the output signal, and yields a DC restored video signal.

Because the output impedance of IC1b is high, and would affect the gain at the non-inverting input of the EL8102, a $47\mu\text{F}$ capacitor (C_2) is used to provide an AC ground and to maintain good high-frequency gain accuracy.

A potentiometer (R_3) is used prior to IC1b to null out any offset voltage contributed by the DC restore circuitry.

Conclusion

The circuit's resultant output is a 200MHz, DC restored video signal in which the sync pulse has been stripped to a residual level of no more than 8mV.

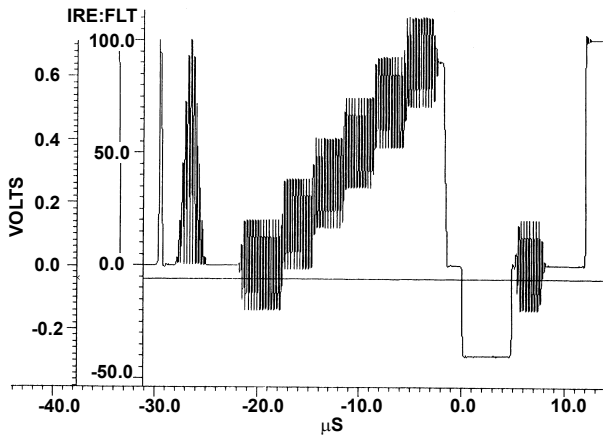


FIGURE 2A. VIDEO AND SYNC GO IN

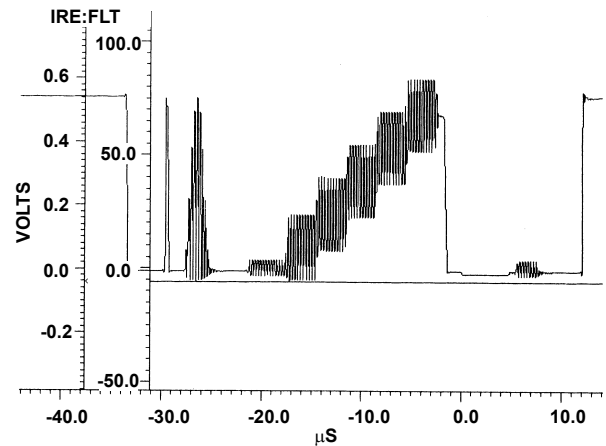


FIGURE 2B. ONLY VIDEO COMES OUT

FIGURE 2. SIGNALS AT EL8102 INPUT AND CABLE OUTPUT

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338